


Agenda

- Administration
- Introduction to Computer Structure
- CMOS Transistors

מבנה מחשבים תרגול 1


תמר נוביק

www.tau.ac.il/~tamarnov/

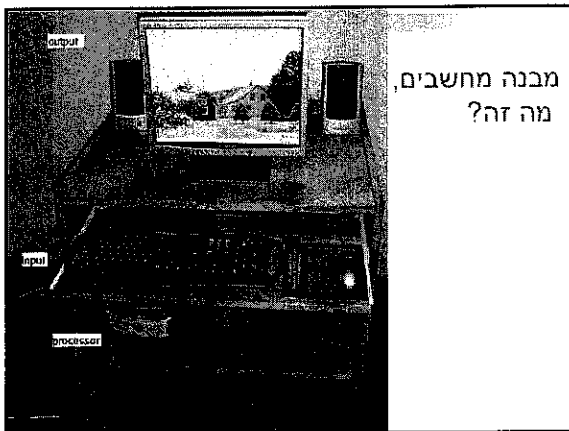


Administration

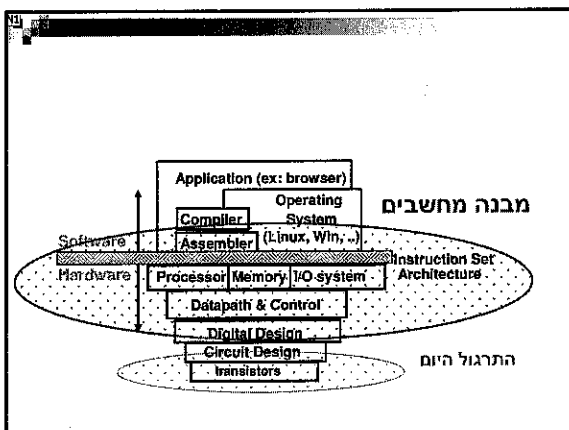- Mail: tamarnov@post.tau.ac.il
- Mailbox: Schreiber 1st floor, box 297
- Homepage: www.tau.ac.il/~tamarnov/comp_struct
- Office hour: Thursday 14:00 – 15:00 (please send me an email in advance)
- Please submit the exercises to the checker's mailbox.
- 7 mandatory exercises
- Exercises Checker:
 - Yaara Tam
 - mailbox: Schreiber 1st floor, box 295




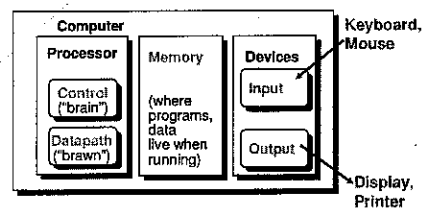Anatomy: 5 components of any Computer (since 1946)



Intel's Core 2 Duo Processor

- 291 Million Transistors

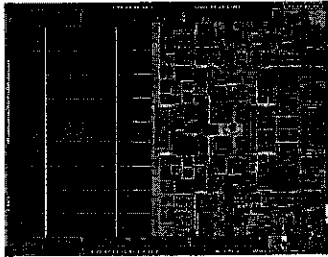

Integrated Circuits (IC)

- Electronic circuit built on a single semiconductor substrate. Also known as a "chip".
- An electric circuit is made from different electrical components such as transistors, resistors and capacitors
- Examples: microprocessor, memory.

מכשיר (מכשיר)
(מכשיר) (מכשיר)
מכשיר (מכשיר)
מכשיר (מכשיר)
(מכשיר) (מכשיר)


Terms

- **Semiconductor (ex: silicon)** - a solid material that has electrical conductivity in between a conductor and an insulator
- **Doping** - is the process of intentionally introducing impurities into an extremely pure semiconductor to change its electrical properties
 - Negatively doped silicon is rich in electrons (negatively charged) and positively doped silicon is rich in holes (the dual of electrons and positively charged)




Transistor

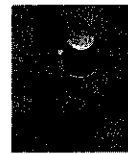- Term derived from "transfer resistor". A semiconductor device commonly used to amplify or switch electronic signals.



MOSFET

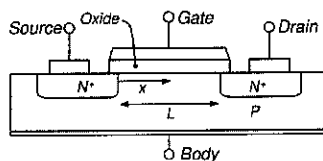- MOSFET = metal-oxide-semiconductor field-effect transistor
- Terminals: *gate*, *drain*, *source* and *body* (/substrate)



CMOS

- Complementary metal-oxide-semiconductor (CMOS)
- Most commonly used integrated circuit
- Uses two types of transistors:
 - N-type transistor (nMOSFET)
 - P-type transistor (pMOSFET)

- switch is closed or 'ON' when drain and source are connected. This occurs when there is a '0' on the GATE

The figure contains four diagrams illustrating PMOS and NMOS transistors:

- PMOS Transistor (Top Left):** A 3D cross-section showing a p-type substrate with an n⁺ source and n⁺ drain. A p⁺ gate is formed by a p⁺ region in the substrate and a p⁺ polysilicon layer on top. An insulator layer covers the top. Labels include: DRAIN, GATE, CONDUCTION, INSULATOR, n⁺ SOURCE, p⁺ POLYSILICON ON SUBSTRATE, and p⁺ TRANSISTOR.
- PMOS Symbol (Top Right):** A circuit symbol for a PMOS transistor. It shows a gate connected to the source and drain. The source is labeled "DRAIN" and the drain is labeled "SOURCE". The substrate is labeled "SUBSTRATE". The symbol is labeled "PMOS SYMBOL".
- NMOS Transistor (Bottom Left):** A 3D cross-section showing a p-type substrate with an n⁺ source and n⁺ drain. A p⁺ gate is formed by a p⁺ region in the substrate and a p⁺ polysilicon layer on top. An insulator layer covers the top. Labels include: DRAIN, GATE, CONDUCTION, INSULATOR, n⁺ SOURCE, p⁺ POLYSILICON ON SUBSTRATE, and n⁺ TRANSISTOR.
- NMOS Symbol (Bottom Right):** A circuit symbol for an NMOS transistor. It shows a gate connected to the source and drain. The source is labeled "DRAIN" and the drain is labeled "SOURCE". The substrate is labeled "SUBSTRATE". The symbol is labeled "NMOS SYMBOL".

ביתר
שחמנה
טרוניסטר
בעזרת
החם וצב
מה-P
אל ה-ח
הסימן
מסמן
כיוון
החשמל.

MOSFET	GATE (turning switch ON)	PASSES
N	1	0
P	0	1

S = Gate
a = Drain
b = Source

(שגסער פיל)
 בית ג' וכו'
 לעביר, וואס

?

OR


1

AND

CMOS Inverter – step 1

Truth Table:

INPUT	OUTPUT
0	1
1	0

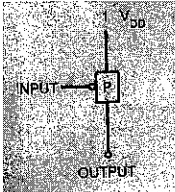


Power Supply

■ 2 power supplies:

- V_{DD} / POWER - "1" = high voltage (5 volts)
- V_{SS} / GROUND - "0" = low voltage (0 volts)

קווי מילוי
 של 5V - V_{DD}
 של 0V - V_{SS}
 סכום 5V + 0V = 5V
 5V + 0V = 5V

NAND Gate

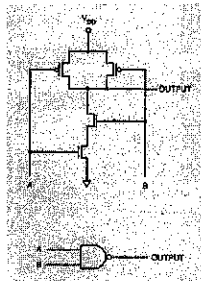


Truth Table:

A	B	Output
0	0	1
1	0	1
0	1	1
1	1	0


1/10
 NAND &
 AND

CMOS Inverter – Step 2

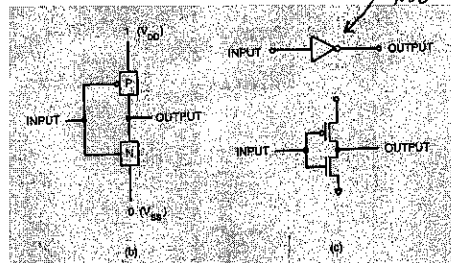


1/10 - V_{DD}
 של 5V - V_{DD}
 של 0V - V_{SS}

AND Gate

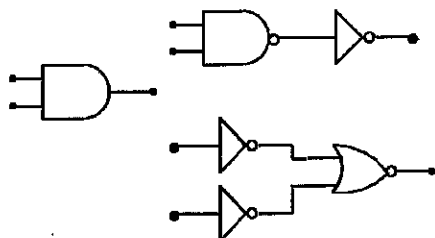

NOR Gate

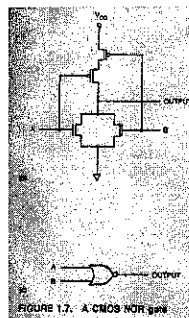

Truth Table:

A	B	Output
0	0	1
1	0	0
0	1	0
1	1	0

Backup

References

- Neil Weste, Karman Eshraghian.
Principles of CMOS VLSI Design.
Addison-Wesley Publishing Company, 1985

IC Pin Layout

